

Gate driver and double pulse tests

 
 


Table of contents

- Primary driver
 - Driver HW dead time
 - Bootstrap circuit
- Double pulse test
 - Setup
 - Example of the pre-processing
 - Rg impact
- Gate current
- Secondary driver
- Annexes
 - Carat of the big Lm
 - Quick prototyping of rogowski coil
 - Double pulse code STM32f103

Primary driver

MosfetGateDriverAndDoublePulseTests

 


Figure 1 Reminder of the primary gate driver sub-schematic: Final version

Driver HW dead time

Let's check the accuracy of the programmed (HW) dead time of the used driver

No SW dead time was programmed, the dead time is managed ONLY by thr RT = 11.5kohm

Oscilloscope:

- **CH1** : INA
- **CH2** : INB

- CH3 : OUTA
- CH4 : OUTB

Driver:

ucc21520Q

Programmed dead time

RT = 11.5k, so dead time = 115ns

 


Figure 2 Zoom out to see 2 periods, 100khz

 


Figure 3 Zoom in around the dead time:
DT=126ns

 


Figure 4 Zoom out to see 2 periods, 100khz

 


Figure 5 Zoom in around the dead time:
DT=116ns

$$DT_{Prog} = 115 \text{ (ns)}$$

$$DT_{Meas} = 116 \text{ (ns)}$$

$$\text{Error} = 100 \cdot \frac{DT_{Meas} - DT_{Prog}}{DT_{Prog}} = 100 \cdot \frac{116 - 115}{115} = 0.87 \text{ (\%)}$$

So the mesured dead time is very accurate

Bootstrap circuit

Lest's check the bootstrap circuit (DRC)

SINGLE pulse

In this test, the low-side MOSFET is driven by a single long pulse.

Peak current estimation :

$$V_{12} = 12 \text{ (V)}$$

$$V_d = 0.700 \text{ (V)}$$

$$R_{boot} = 2.150$$

$$I_{boot} = \frac{V_{12} - V_d}{R_{boot}} = \frac{12 - 0.700}{2.150} = 5.256$$

 


Figure 6 Bootstrap circuit measurement with 10us pulse width

Oscilloscope:

- **CH1** : bootstrap capacitor voltage
- **CH2** : bootstrap diode current
- **CH4** : Vgs low side MOSFET

Peak current measurement :

$$I_{bootMeasure} \sim 3.8 A_{peak}$$

The measured peak current is lower than the estimated value because the estimate was based on the assumption that the only resistance in the path was the 2.15-ohm resistor, which represents a pessimistic (worst-case) assumption.

Below is a fast/simplified reproduction of this test in simulation

 


Figure 7 Quick simulation of the bootstrap circuit with 10us pulse width

PWM mode

In this test, the low-side MOSFET is driven by a pulse train with frequency of 100kHz (more realistic).

 


Figure 8 Bootstrap circuit measurement with PWM 100kHz 50% duty cycle

Below is a fast/simplified reproduction of this test in simulation

 


Figure 9 Quick simulation of the bootstrap circuit 100kHz 50% duty cycle

Estimation of the charge time of the bootstrap capacitor:

$$C = 1 \text{ } (\mu\text{s})$$

$$R = 2.150 \text{ (ohm)}$$

$$T_o = R \cdot C = 2.150 \cdot 1 = 2.150 \text{ } (\mu\text{s})$$

3 corresponds to the 99% level, and 2 represents the 50% duty cycle.

$$\text{time} = T_o \cdot 5 \cdot 2 = 2.150 \cdot 5 \cdot 2 = 21.500 \text{ } (\mu\text{s})$$

So minimum time to charge the capacitor is 22μs or 3 perodes of 100khz

Double pulse test

Setup

We used the primary side of the DC-DC (without ferrite elements) to make the double pulse test.

 


Figure 10 Double pulse setup

 


Figure 11 Double pulse setup (with the big inductance 360μH, 16 turns)

Example of the pre-processing

In this section an example of pre-processing measured signal to calculate the E_{on} , and E_{off} energy

Step 1: Load the csv files


 



Figure 12 Quick simulation of the bootstrap circuit with 10µs pulse width

 


Step 2 : Pre-processing the current

The used current prob has a heigh pass filter effect, so below a pre-processing to remove this effect.

 Correction of the current of ID: remove the heigh pass filter effect of the sensor




 Step 3: Detection of the rise/fall instants




Step 4: zoom around the switching instants

 Pre-Processed data of turn off/on instants, DC-bias = 366.5V



Step 5: Estimation of the Coss capacitor

 

Formulas to calculate the mosfet capacitors:

Time related capacitance


$$i = C \frac{dv}{dt}$$

$$C_o(tr) = \frac{\int i \cdot dt}{\int dv} = \frac{Q}{\Delta V}$$

Energy-related capacitance

$$E = \int v \cdot i \cdot dt$$

$$C_{o(er)} = \frac{2E}{\Delta V^2}$$

 

Why the estimation of Co-Energy is good at low current, and bad in heigh current:

$$E_{total} = E_{oss} + E_{switching_loss}$$

In low current loss energy is low so almost the all measured energy is the stored energy in the mosfet capacitor, but in heigh current a part of energy is converted to heat.

To reproduce this phynomina, I propose the simple simulation below:



 


Figure 13 Simple simulation of the turning off instant of SPA11N60C3

Lest's calculating the sw-engry and the coresponding capacitor using pre-processing of the raw data using python
 
```
Text(0.5, 1.0, 'Switching power = Id * Vds (W)')
```



 

So , we can see the same behaviour our measurement

time	V(m)*Id(M1)
0	0.0 -0.0
1	0.0 -0.0
2	0.0 -0.0
3	0.0 -0.0
4	0.0 -0.0

Rg impact

In this section, we will change gate resistor, and check the impact in the loss energy.

We calculating the Eon just for information, since we are in ZVS, Eon is very low, and the calculated Eon is compatible with no ZVS function.

In the PCB we mount 3 resistors in parallel for Rg, 3 Ω , 5 Ω and 10 Ω with a jumper, so it will be easy to change Rg using this value, or any combinason of parallel configuration like 3 Ω // 5 Ω = 1.875 Ω and 3 Ω // 10 Ω =2.30 Ω (see the photo below)

Just for information, we broked the mosfet during this test @400V, so we recommande to no make SW-ON.

 


Figure 14 The Jumper used to select R_g


 


Figure 15 Jumper in the PCB with the 3 resistors (3D)

 We followed the same steps as shown in the example above to calculate the E_{on}/E_{off} of each R_g configuration



$R_g = 3 \Omega$ is a good compromise between reducing the switching energy and avoiding oscillation, we will conserve this value for this project

Gate current

In this test, we measured the gate current using TCP202, so a small loop wire is added to the current path to insert the current probe (inductance)

The test was done in low voltage condition:

- $V_{in} = 48.03V$
- $V_{out} = 8.03V$
- $Freq = 150kHz$ (Max freq of the DC-DC)

This test is done with the old primary mosfet (before updating the BOM)


 
 


Figure 16 Primary-Low side gate current/voltage

 Pre-Processing of the oscilloscope raw data



MOSFET: Miller plateau

Turn ON, gatecharge Mosfet IPW60R037CM8XKSA1, $V_{dd} = 11.35V$ 

The Miller plateau is not very pronounced because the SW-ON is in ZVS mode and at low voltage.

Secondary driver

Reminder of the secondary-side synchronous rectifier driver

the master ic : NCP43080DDR2G

 


Figure 17 The driver NCP43080DDR2G

 


Figure 18 Jumper to shose R_g from 0, 1, 3 ohm

The controller presents a limitation, its conduction time depends heavily on the load; see the test below.

Test conditions:

- $V_{in} = 393.5 \text{ V}$
- $V_{out} = 48.11 \text{ V}$

Oscilloscope:

- CH1 : V_{ds} low side primary x 100
- CH2 : V_{gs} low side secondary: driver output
- CH4 : V_{ds} low side secondary x 10

 


Figure 19 no load

 


Figure 20 load1 52.1 ohm

 


Figure 21 load2 36 ohm

 


Figure 22 load3 3 24.5 ohm

 


Figure 23 load4 12.8 ohm

 


Figure 24 load5 9.2 ohm

Grouping of all test data :

 


Figure 25 PreProcessing of the test results

Annexes

Carat of the big Lm

 


Figure 26 Current

 


Figure 27 Voltage

We used the same double-pulse setup to characterize the large 16-turn inductor.

See the oscilloscope above (CH1 is and isolated x 100 prob)

$$\begin{aligned}
 N &= 16 \text{ (turns)} \\
 \Delta_I &= 1.820 \text{ (A)} \\
 \Delta_t &= 7.360 \text{ (}\mu\text{s)} \\
 V_L &= 928 \cdot 100 \cdot 1 \times 10^{-3} = 92.800 \text{ (V)}
 \end{aligned}$$

$$\text{Since } V_L = L \frac{di}{dt}$$

$$L = V_L \cdot \left(\frac{\Delta_t}{\Delta_I} \right) = 92.800 \cdot \left(\frac{7.360}{1.820} \right) = 375.279 \text{ (}\mu\text{H)}$$

$$AL = 1 \times 10^3 \cdot \frac{L}{(N)^2} = 1 \times 10^3 \cdot \frac{375.279}{(16)^2} = 1465.934 \text{ (nH/turn}^2\text{)}$$

Quick prototyping of rogowski coil

During this project, we experimented with several methods to produce a prototype of a Rogowski coil, The idea is to prototype a very simple Rogowski coil and perform the integration via signal preprocessing.

the produced signal is:

$$e = k \cdot di/dt$$

So a preprocessing integral is necessary and an empirical estimation of the coed k

Below some image of the prototyped coils:

 


Figure 28

 


Figure 29

 


Figure 30

 


Figure 31

 


Figure 32



Figure 33

 


Figure 34

 


Figure 35

lek Stop

Ch1 High 2.84 V


Ch4 Pk-Pk 4.25 V


5 Aug 2025 21:30:15

 4.00000ns

21

- CH3 is TCP202 360 μ H current
- CH4 Rogowski coil voltage (terminal 50ohm)



 

Preprocessed rogowski signal is very good to detect fast change of the current but bad in low frequency area

Double pulse code STM32f103

Simple double pulse code

```
#include "stm32f1xx.h"

#define CPU_FREQ 72000000UL
#define PA9_SET (1u << 9)
#define PA9_RST (1u << (9 + 16))
#define PA9_BIT (1u << 9)

static inline void dwt_start(void) {
    CoreDebug->DEMCR |= CoreDebug_DEMCR_TRCENA_Msk;
    DWT->CYCCNT = 0;
    DWT->CTRL |= DWT_CTRL_CYCCNTENA_Msk;
}

void setup(void) {
    // Enable GPIOA clock
    RCC->APB2ENR |= RCC_APB2ENR_IOPAEN;

    // PA9 = General purpose push-pull output, 50 MHz (CRH bits [7:4])
    GPIOA->CRH &= ~(0xFu << 4);
    GPIOA->CRH |= (0x3u << 4); // MODE9=11 (50MHz), CNF9=00 (GP PP)
```

```

// Ensure USART1 doesn't grab PA9 (we don't enable it)
RCC->APB2ENR &= ~RCC_APB2ENR_USART1EN;

dwt_start();

// Quick self-check: force LOW and verify ODR reflects it
GPIOA->BSRR = PA9_RST;
if (GPIOA->ODR & PA9_BIT) { for (;;){ /* trap if config failed */ } }
}

void loop(void) {
    uint32_t ton1 = 2; // us
    uint32_t toff1 = 1; // us
    uint32_t ton2 = 1; // us
    uint32_t toff2 = 1; // us

    GPIOA->BSRR = PA9_SET;
    delayMicroseconds(ton1);

    GPIOA->BSRR = PA9_RST;
    delayMicroseconds(toff1);

    GPIOA->BSRR = PA9_SET;
    delayMicroseconds(ton2);

    GPIOA->BSRR = PA9_RST;
    delayMicroseconds(toff2);
}

```

Train of double pulse

```

#include "stm32f1xx.h"

// --- PA9 macros ---
#define PA9_SET    (1u << 9)
#define PA9_RST    (1u << (9 + 16))

// --- PB14 macros ---
#define PB14_SET   (1u << 14)
#define PB14_RST   (1u << (14 + 16))

#define _Ena_drv  PB10
#define _Dis_drv  PB12

void setup() {
    // Force PB12 HIGH in output data register BEFORE pinMode changes the mode
    // digitalWrite(_Dis_drv, HIGH);      // preload ODR = 1 (float high in
    // open-drain mode)
    digitalWrite(_Dis_drv, LOW);
    pinMode(_Dis_drv, OUTPUT_OPEN_DRAIN);
    digitalWrite(_Dis_drv, LOW); // redundancy
    digitalWrite(_Ena_drv, HIGH);
    pinMode(_Dis_drv, OUTPUT);
    digitalWrite(_Ena_drv, HIGH);
}

```

```

////////// PA9 & PB14 as Fast output //////////
// Enable GPIOA + GPIOB clocks
RCC->APB2ENR |= RCC_APB2ENR_IOPAEN | RCC_APB2ENR_IOPBEN;

// --- PA9 = 50 MHz push-pull output ---
GPIOA->CRH &= ~(0xF << 4); // clear config bits
GPIOA->CRH |= (0x3 << 4); // MODE9=11 (50MHz), CNF9=00
GPIOA->BSRR = PA9_RST; // start LOW

// --- PB14 = 50 MHz push-pull output ---
GPIOB->CRH &= ~(0xF << 24); // PB14 config bits
GPIOB->CRH |= (0x3 << 24); // MODE14=11, CNF14=00
GPIOB->BSRR = PB14_RST; // start LOW

}

```

```

__attribute__((always_inline))
static inline void delayNs(uint32_t tns)
{
    /*
    target => oscilo
    6000ns => 5986ns
    1000ns => 985.3ns
    */

    uint32_t iterations = (tns * 72) / (6.08*1000);

    for (uint32_t i = 0; i < iterations; i++) {
        __asm__ __volatile__("nop" ::: "memory");
    }
}

```

```
void loop() {
```

```

////////// ENABLE DRIVER
delayMicroseconds(10);
digitalWrite(_Dis_drv, HIGH); // redundancy
digitalWrite(_Ena_drv, LOW);
delayMicroseconds(10);
digitalWrite(_Ena_drv, HIGH);

////////// double pulse waveform on / off / on /off

uint32_t ton = 1000; // ns

```

```
uint32_t toff = 800; // ns
uint32_t N = 17; // n of pulses

for (int i = 0; i<N; i++){
    GPIOA->BSRR = PA9_SET;
    delayNs(ton);
    GPIOA->BSRR = PA9_RST;
    delayNs(toff);
}

while(1);

}
```